 




**POLITECNICO**  
MILANO 1863



**OrCAD**<sup>TM</sup>  
CADENCE PCB SOLUTIONS

**CAD circuit simulation project**


**Ex.3 from 200909 exam**

**Student:** Martin Molinaro (991671)

1 2 3 1033 1034


Consider an 8bit DAC and a dual OpAmp.

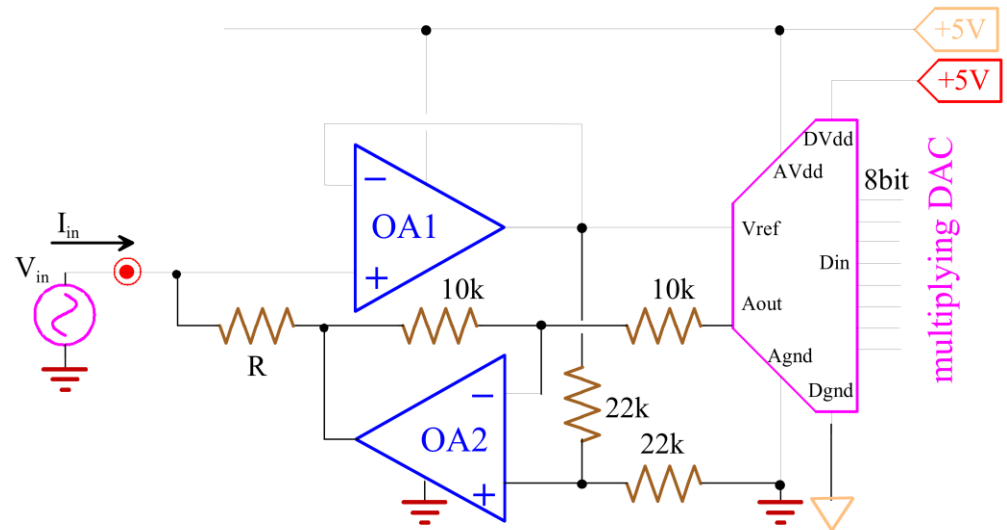- Compute the  $V_{in}(I_{in})$  relationship dependence on the digital input code  $D_{in}$  and the R resistor.
- Substitute the DAC with an 8bit ADC (i.e.  $A_{out}$  becomes  $A_{in}$  and  $D_{in}$  becomes  $D_{out}$ ) and write  $D_{out}$  as a function of  $V_{in}$ .



Solution by hand:

a)

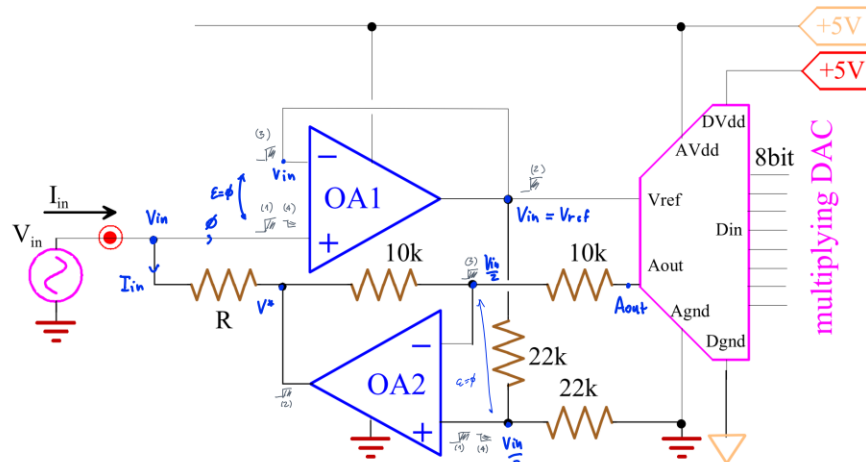

$$\Rightarrow I_{in} = \frac{V_{in} - V^+}{R} = \frac{V_{in} - V_{in} + \frac{V_{in} \frac{D_{in}}{2^8} A_{out}}{R}}{R} = \frac{V_{in} D_{in}}{2^8 \cdot R} + \frac{A_{out}}{R}$$

$$\hookrightarrow V_{in} = \frac{2^8 R I_{in}}{D_{in}}$$

(negative feedback)

$$\bullet I_{in} = \frac{V_{in} - V^+}{R}$$

$\bullet V^+ \rightarrow$  Superposition effect

①  $V_{in}$  ON,  $A_{out}$  OFF

$$V^+ = \frac{V_{in}}{2} \left( 1 + \frac{10k}{10k} \right) = V_{in}$$

②  $V_{in}$  OFF,  $A_{out}$  ON


$$V^+ = A_{out} \left( -\frac{10k}{10k} \right) = -A_{out}$$

$$\hookrightarrow V^+ = V_{in} - A_{out} = V_{in} - V_{in} \frac{D_{in}}{2^8}$$

$$\bullet \text{DAC: } A_{out} = V_{ref} \frac{D_{in}}{2^8} = V_{in} \frac{D_{in}}{2^8}$$


# ES3a

## OrCAD circuit scheme

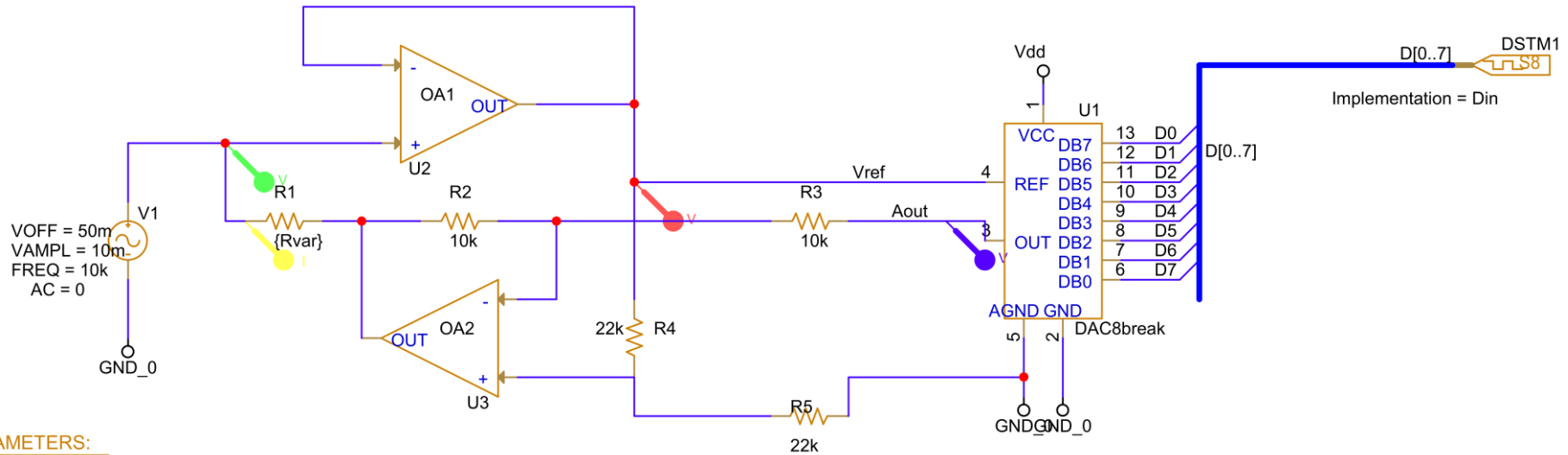


### PARAMETERS:

Rvar = 1k

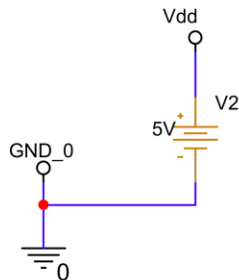


### Given schematics

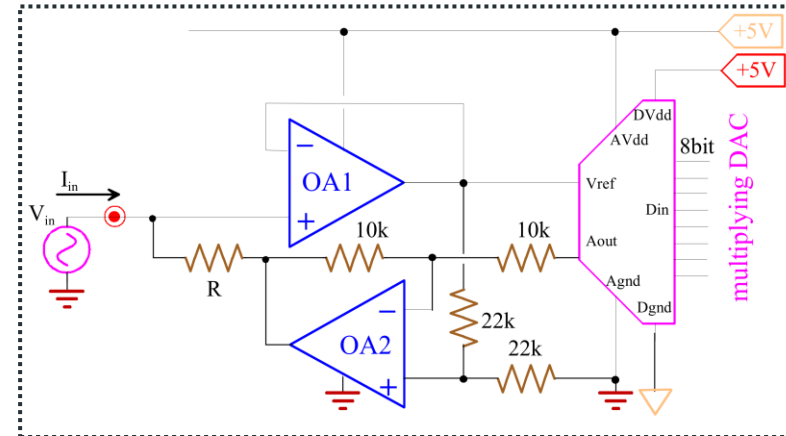

# ES3a


## Digital Input stimulus

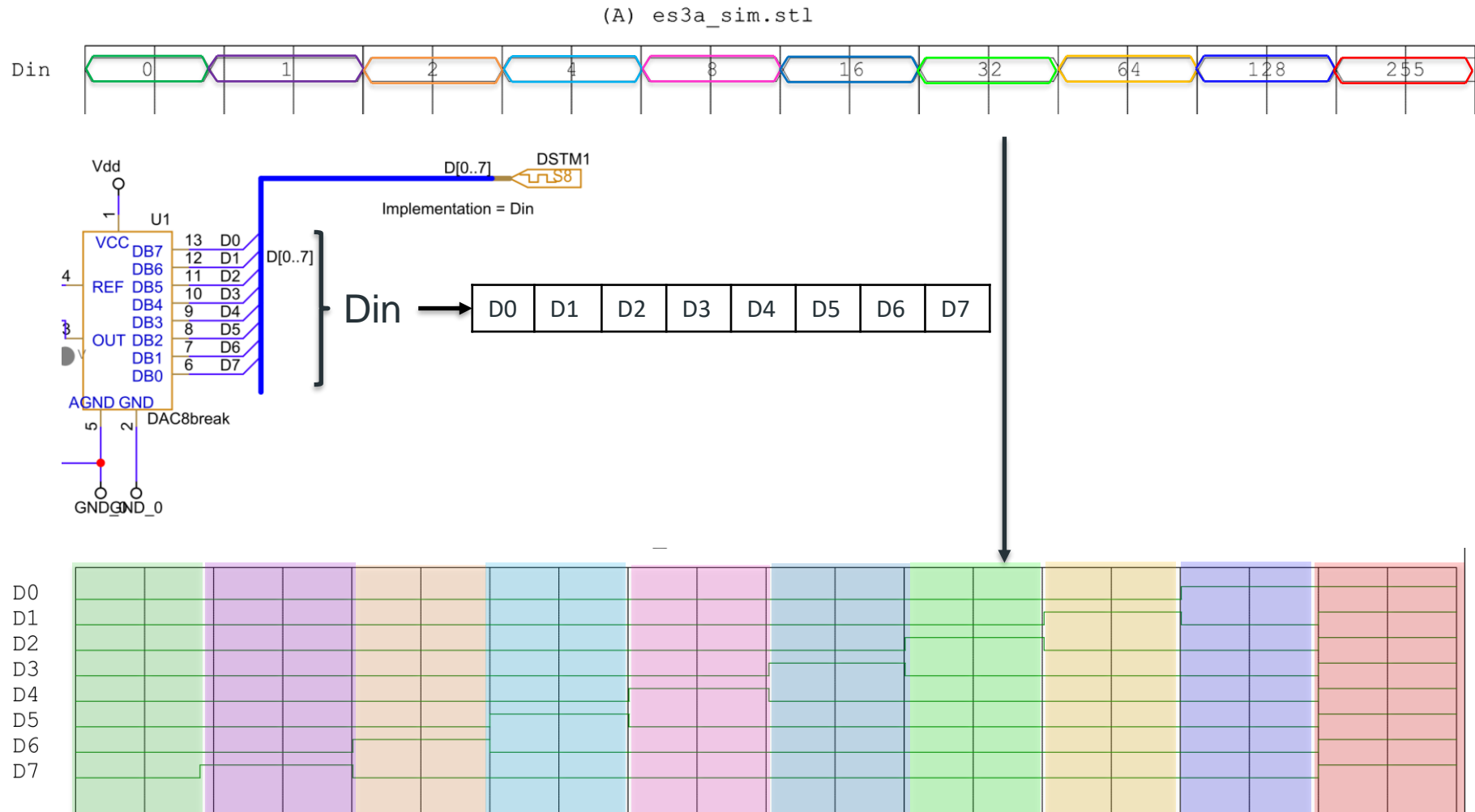

# ES3a
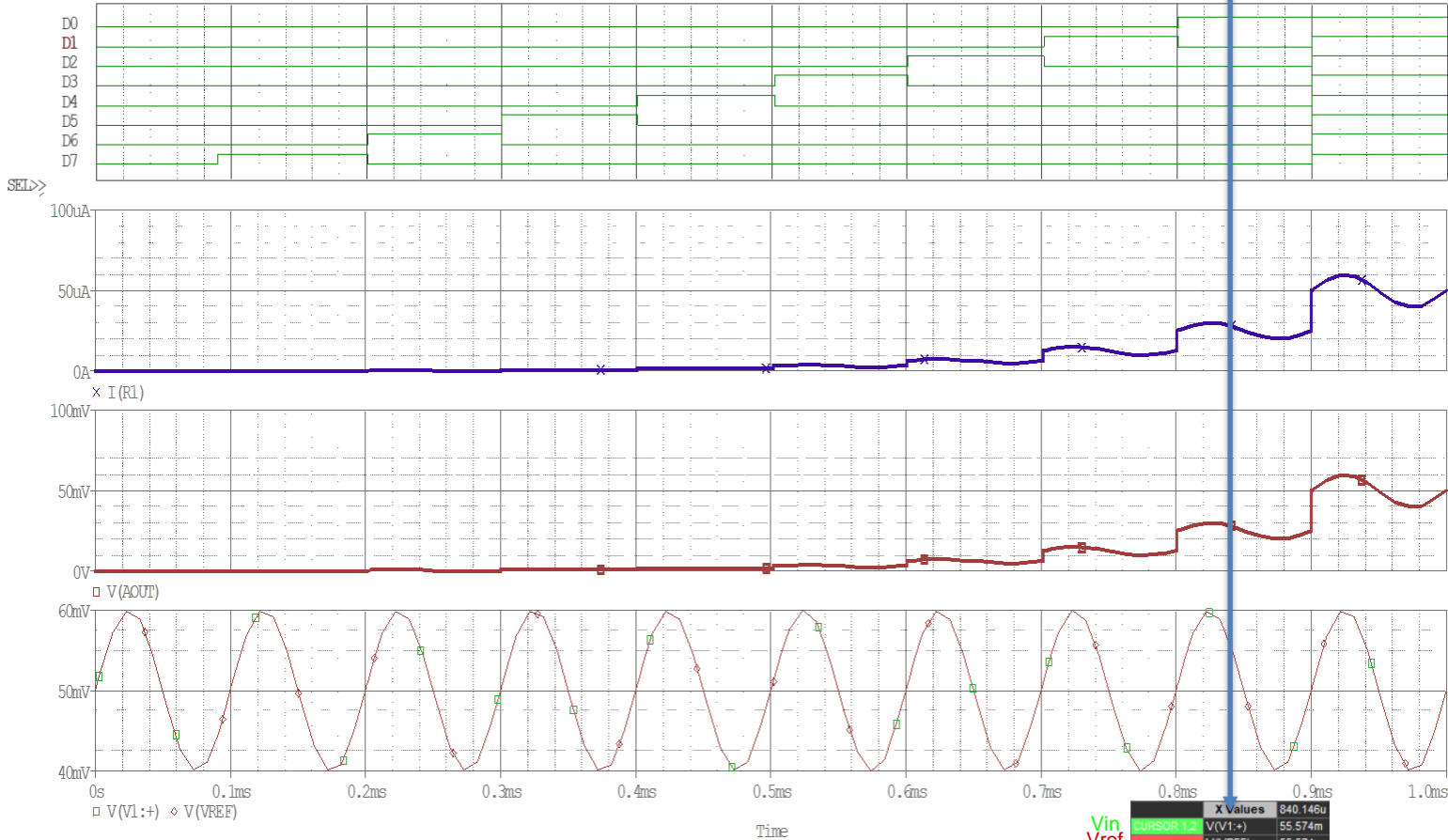
## Simulation Results

(simulation: es3a\_sim) with  $R(R1)=1k\Omega$



Din

Iin

Aout

Vin = Vref

• DAC:  $A_{out} = V_{ref} \frac{D_{in}}{2^8} = V_{in} \frac{D_{in}}{2^8}$   
 $\uparrow$   
 $= V_{in}$

X Values	840.146u
CURSOR 1,2	55.574m
V(V1:+)	55.574m
V(VREF)	55.574m
V(AOUT)	27.787m
I(R1)	27.787u


Vin  
Vref  
Aout  
Iin  
Din=2<sup>7</sup> = 128

$$\frac{V_{ref} D_{in}}{2^8} = \frac{V_{in} D_{in}}{2^8} = \frac{V_{in} 2^7}{2} = \frac{V_{in}}{2} = \frac{55.574m}{2} = 27.787m$$

# ES3a
 
## Simulation Results

(simulation: es3a\_sim) with  $R(R1)=1k\Omega$



CURSOR 1,2	V(AOUT)	161.436u
	I(R1)	161.559n

\*R(R1)=1kΩ

$$I_{in} = \frac{V_{in} - V^+}{R} = \frac{V_{in} - V_{in} + V_{in} \frac{A_{out}}{2^8}}{R} = \frac{V_{in} \frac{A_{out}}{2^8 \cdot R}}{R} = \frac{A_{out}}{R}$$

Aout


Vin , Vref

V(V1: +)	41.301m
V(VREF)	41.301m

# ES3a

## Simulation Results

(simulation: es3a\_sim) with R(R1)=5kΩ

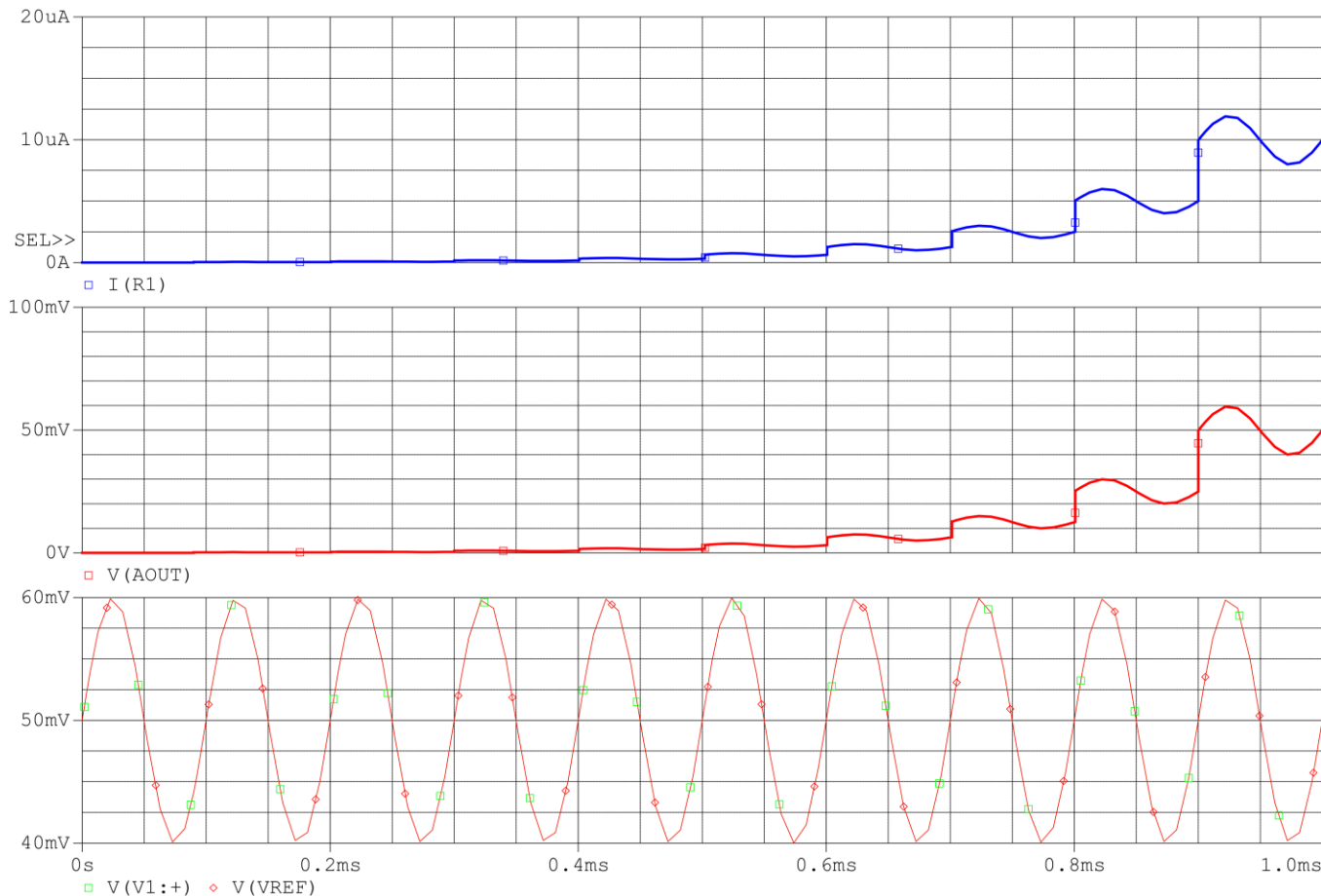

V(AOUT)	1.5096m
CURSOR 1,2 I(R1)	301.945n

\*R(R1)=5kΩ

lin

$$I_{in} = \frac{V_{in} - V^+}{R} = \frac{V_{in} - V_{in} + \frac{A_{out} D_{in}}{2s}}{R} = \frac{V_{in} D_{in}}{2s \cdot R} = \frac{A_{out}}{R}$$

Aout

Vin , Vref


V(V1: +)	48.293m
V(VREF)	48.293m



# ES3a
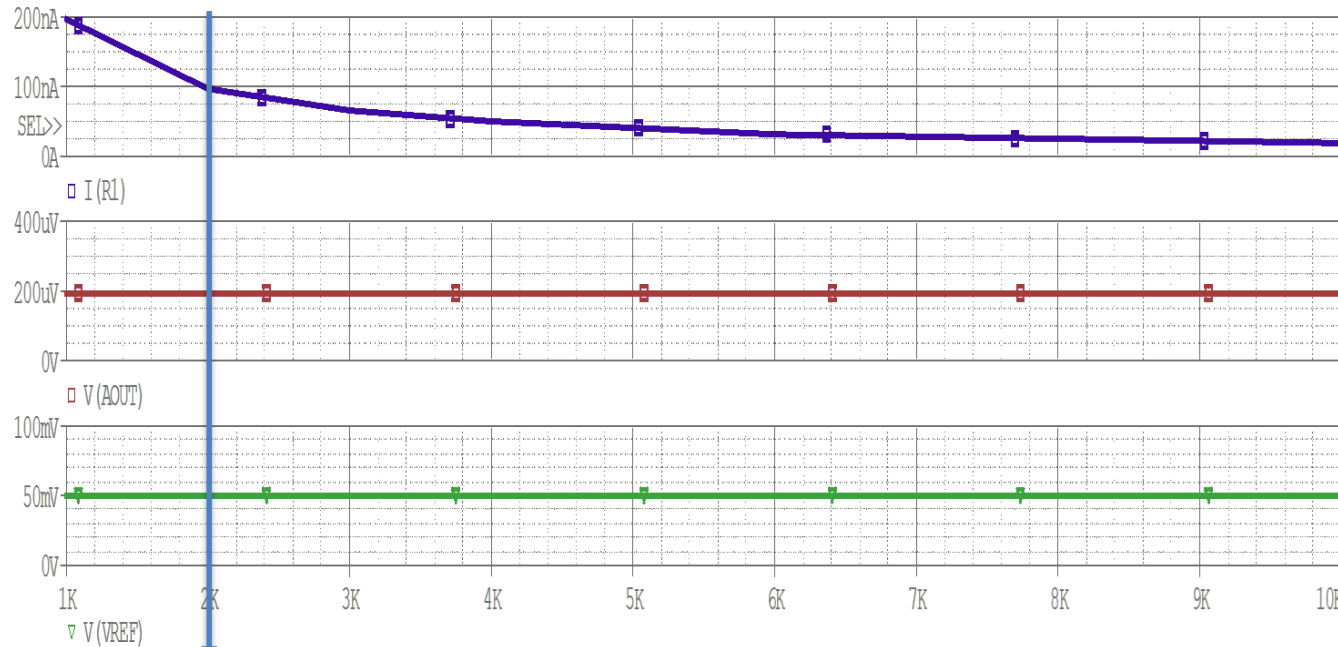
## Simulation Results

(simulation: es3a\_sweep) with R(R1)=Rvar=[1kΩ÷10kΩ], Din=1 constant, Vin=Vref=50mV (constant bias)



$I_{in}$

$$A_{out} = \frac{V_{ref} D_{in}}{2^8} = \frac{V_{ref} \cdot 1}{256} = \frac{50mV \cdot 1}{256} = 195.312\mu V$$


$V_{ref}$

Trace Color	Trace Name	Y1
	X Values	2.0000K
	V(VREF)	50.000m
	V(AOUT)	195.312u
CURSOR 1,2	I(R1)	97.731n

$$I_{in} = \frac{A_{out}}{R} = \frac{195.312\mu V}{2k\Omega} = 97.7nA$$

$$I_{in} = \frac{V_{in} - V^+}{R} = \frac{V_{in} - V_{in} + \sqrt{V_{in} \frac{D_{in}}{2^8}}}{R} = \frac{V_{in} D_{in}}{2^8 \cdot R} = \frac{A_{out}}{R}$$

$V_{ref}$   
 $A_{out}$   
 $I_{in}$

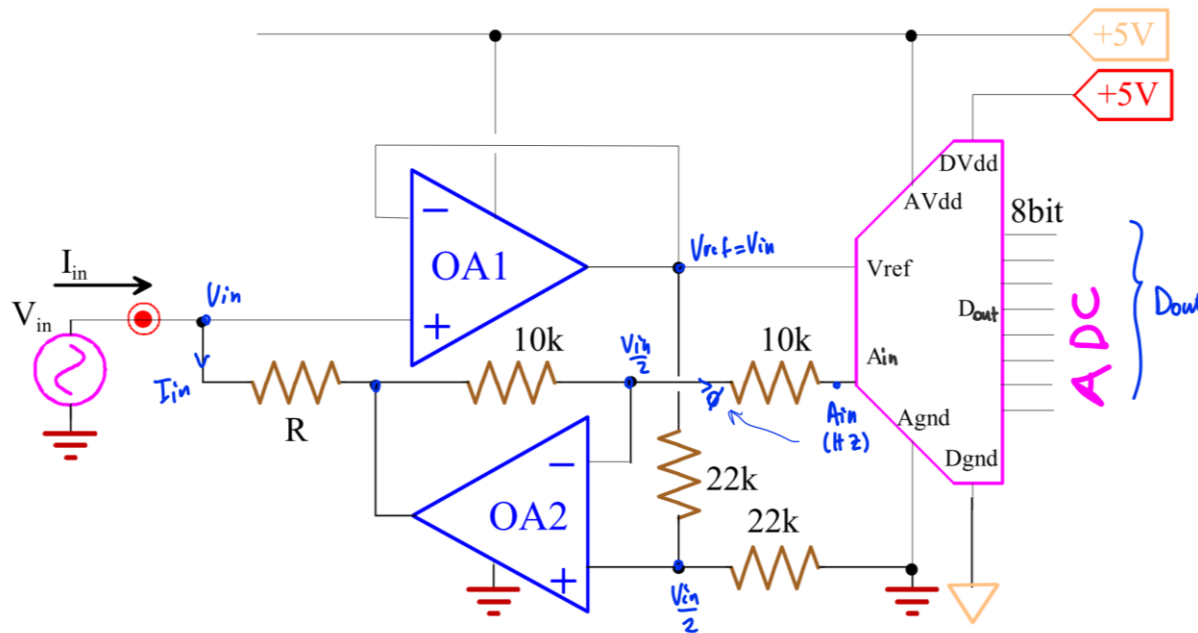


$$A_{in} = \frac{V_{in}}{2}, \quad V_{ref} = V_{in}$$

$$D_{out} = \frac{A_{in}}{\frac{V_{ref}}{2^8}} = \frac{\frac{V_{in}}{2}}{\frac{V_{in}}{2^8}} = 2^7$$

# ES3b

## OrCAD circuit scheme

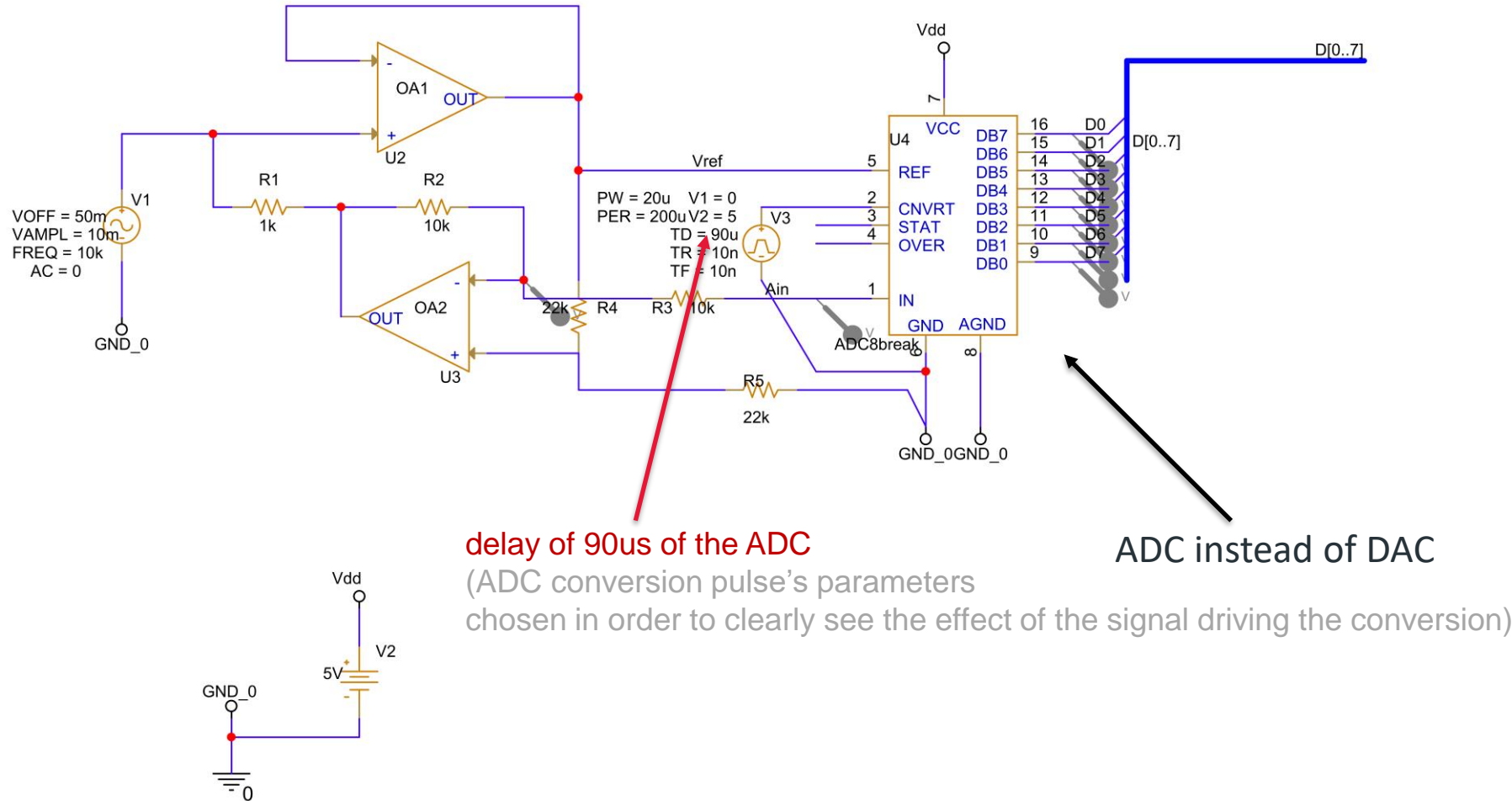




# ES3b

## Simulation Results

(simulation: es3b\_sim) with  $R(R1)=1k\Omega$  delay of 90us of the ADC

$$Dout=1000000=2^7$$

D0	D1	D2	D3	D4	D5	D6	D7
----	----	----	----	----	----	----	----

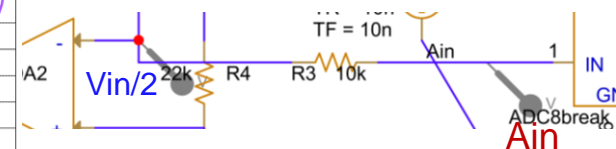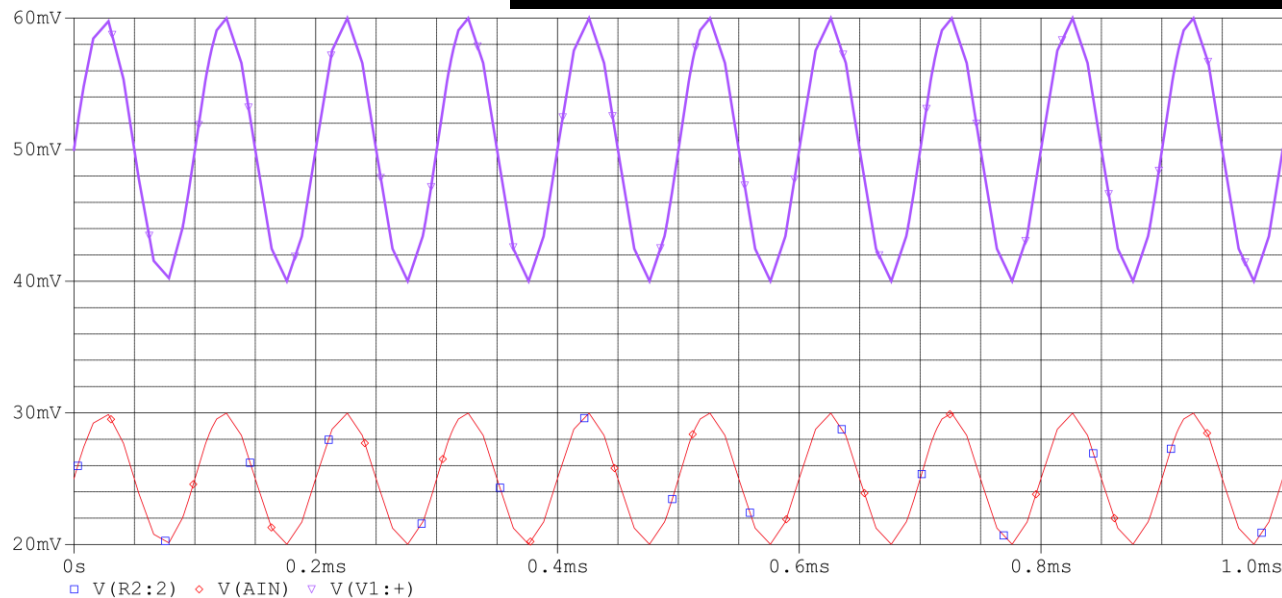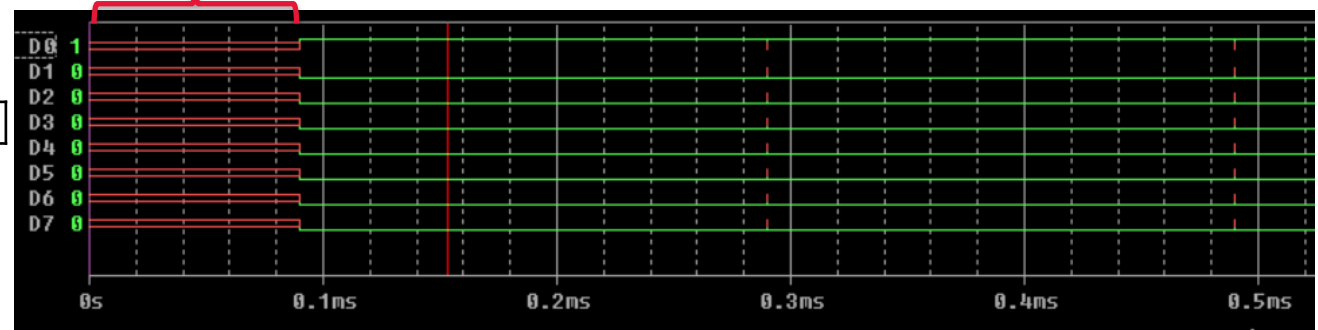

$V_{in}$  ,  $A_{in}$  ,  $V_{in}/2$

CURSOR 1,2	V(R2:2)	22.491m
	V(AIN)	22.491m
	V(V1:+)	44.908m